 
 

CMOS INVERTER




The Ideal Gate




$$R_i = \infty$$

$$R_o = 0$$

 
DC Operation: Voltage Transfer Characteristic




CMOS Inverter VTC

 

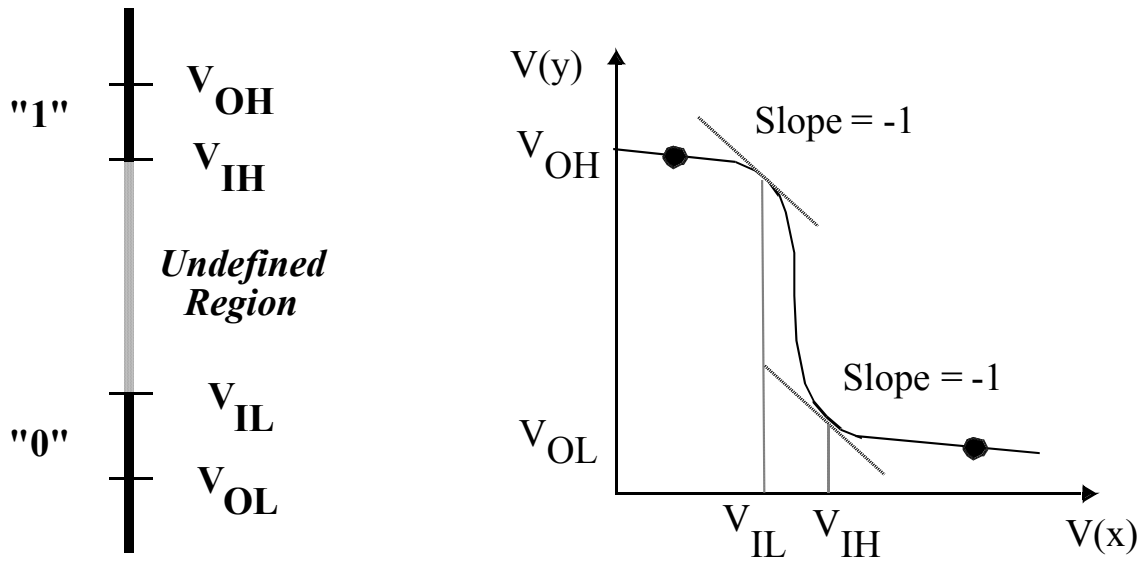
Mapping between analog and digital signals




Definition of Noise Margins

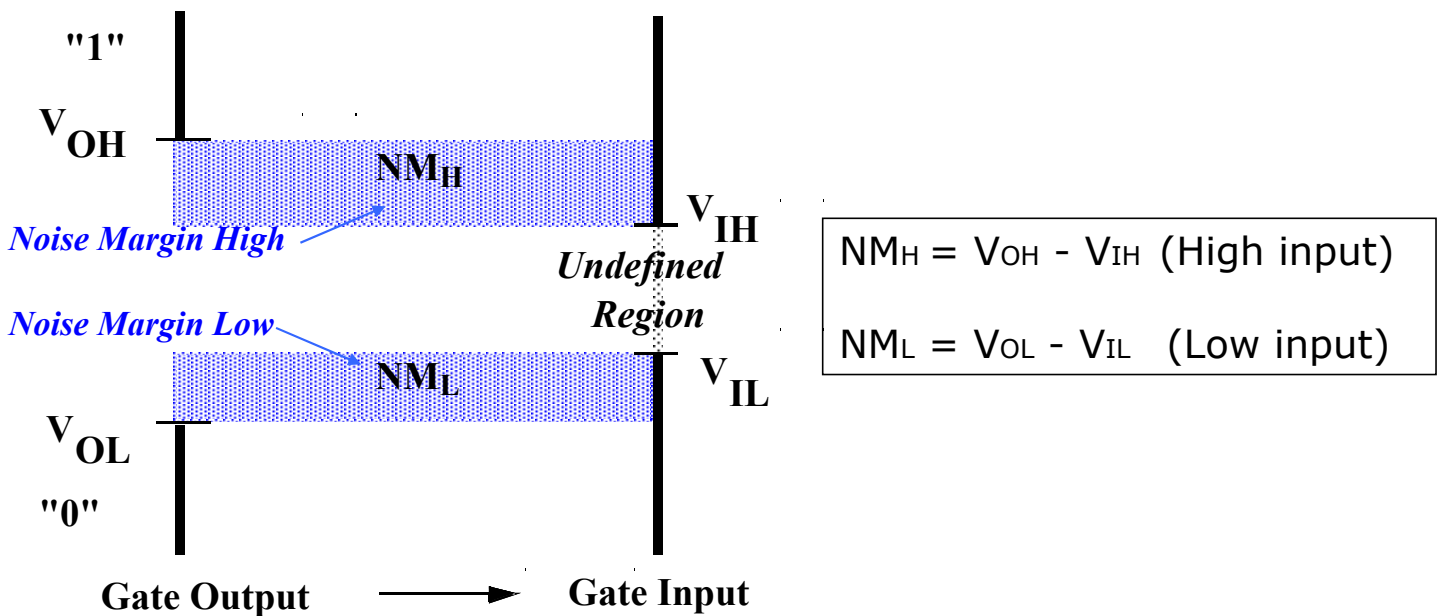


Fan-in and Fan-out

 


The CMOS Inverter: A First Glance

 


Delay Definitions

 


CMOS Inverters

 


Switch Model of CMOS Transistor

 


CMOS Inverter: Steady State Response

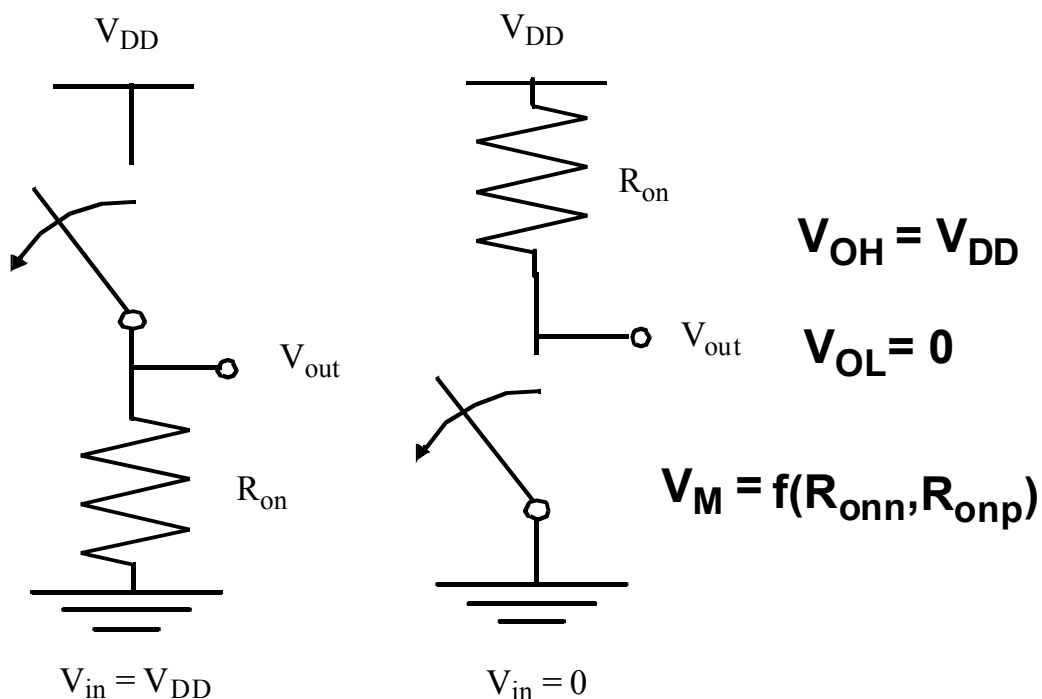


CMOS Inverter: Transient Response

 


CMOS Inverter Propagation Delay

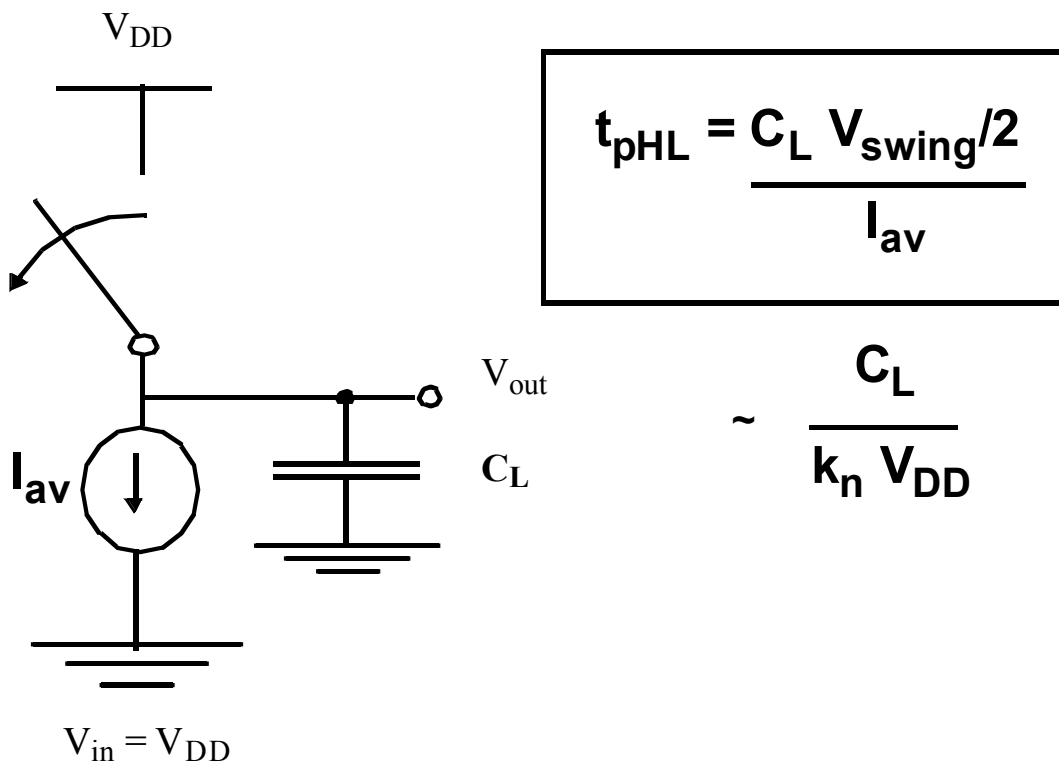

Dynamic Behavior of MOS Transistor

 

The Gate Capacitance

 

$$C_{gate} = \frac{\epsilon_{ox}}{t_{ox}} WL$$


Average Gate Capacitance

Different distributions of gate capacitance for varying operating conditions

Operation Region	C_{gb}	C_{gs}	C_{gd}
Cutoff	$C_{ox}WL_{eff}$	0	0
Triode	0	$C_{ox}WL_{eff}/2$	$C_{ox}WL_{eff}/2$
Saturation	0	$(2/3)C_{ox}WL_{eff}$	0

Most important regions in digital design: saturation and cut-off


Diffusion Capacitance

 

$$C_{diff} = C_{bottom} + C_{sw} = C_j \times AREA + C_{jsw} \times PERIMETER$$

$$C_{diff} = C_j L_S W + C_{jsw} (2L_S + 2W)$$

Junction Capacitance

 

$$C_j = \frac{C_{j0}}{(1 - V_D/\phi_0)^m}$$


Linearizing the Junction Capacitance

Replace non-linear capacitance by
large-signal equivalent linear capacitance
which displaces equal charge
over voltage swing of interest

$$C_{eq} = \frac{\Delta Q_j}{\Delta V_D} = \frac{Q_j(V_{high}) - Q_j(V_{low})}{V_{high} - V_{low}} = K_{eq} C_{j0}$$


$$K_{eq} = \frac{-\phi_0^m}{(V_{high} - V_{low})(1 - m)} [(\phi_0 - V_{high})^{1-m} - (\phi_0 - V_{low})^{1-m}]$$

The Miller Effect

 

“A capacitor experiencing identical but opposite voltage swings at both its terminals can be replaced by a capacitor to ground, whose value is two times the original value.”

Computing the Capacitances

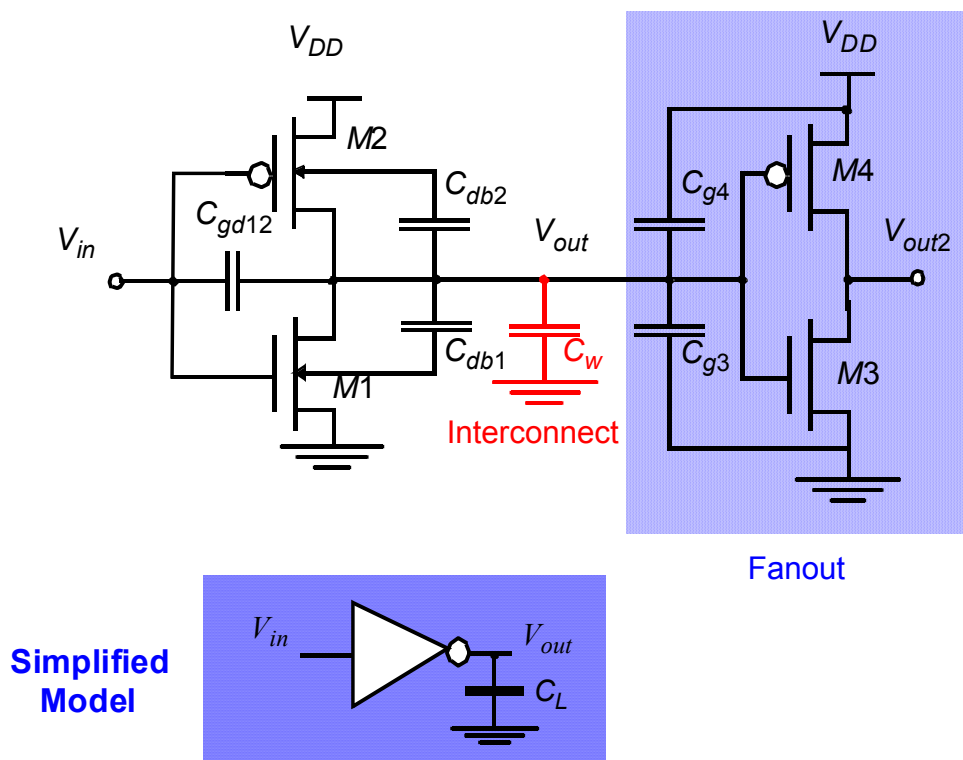

Computing the Capacitances

Capacitor	Expression
C_{gd1}	$2 C_{GD0} W_n$
C_{gd2}	$2 C_{GD0} W_p$
C_{db1}	$K_{eqn} (AD_n C_J + PD_n C_{JSW})$
C_{db2}	$K_{eqp} (AD_p C_J + PD_p C_{JSW})$
C_{g3}	$C_{ox} W_n L_n$
C_{g4}	$C_{ox} W_p L_p$
C_w	From Extraction
C_L	Σ

Capacitances: Typical values

Table 3.5 Capacitance parameters of NMOS and PMOS transistors in 0.25 μm CMOS process.

	C_{ox} (fF/ μm^2)	C_o (fF/ μm)	C_j (fF/ μm^2)	m_j	ϕ_b (V)	C_{jsw} (fF/ μm)	m_{jsw}	ϕ_{bsw} (V)
NMOS	6	0.31	2	0.5	0.9	0.28	0.44	0.9
PMOS	6	0.27	1.9	0.48	0.9	0.22	0.32	0.9