
 


DC Current in CMOS

- > For $V_{IN} < V_{TN}$, N_O is cut off and $I_{DD} = 0$.
- > For $V_{TN} < V_{IN} < V_{DD}/2$, N_O is saturated.
- > For $V_{DD}/2 < V_{IN} < V_{DD} + V_{TP}$, P_O is saturated.
- > For $V_{IN} > V_{DD} + V_{TP}$, P_O is cut off and $I_{DD} = 0$.
- For $V_{DD}/2 < V_{IN} < V_{DD} + V_{TP}$, P_O is saturated.
- For $V_{IN} > V_{DD} + V_{TP}$, P_O is cut off and $I_{DD} = 0$.
- > Even though CMOS exhibits negligible DC dissipation in either logic state, appreciable power is dissipated during switching.

 

Digital Integrated Circuits

Inverter

© Prentice Hall 1995

Power dissipation in CMOS




- **Dynamic Power Consumption**
Charging and Discharging Capacitors
- **Short Circuit Currents**
Short Circuit Path between Supply Rails during Switching
- **Leakage**
Leaking diodes and transistors

Digital Integrated Circuits

Inverter

© Prentice Hall 1995

Dynamic Power Dissipation

   

Capacitor Energy:

$$E_C = 1/2 C V_{dd}^2$$

Digital Integrated Circuits

Inverter

© Prentice Hall 1995

Dynamic Power Dissipation

For each transition (clock cycle):

$$\text{Energy/transition} = C_L * V_{dd}^2$$

$$\text{Power} = \text{Energy/transition} * f = C_L * V_{dd}^2 * f$$

- Not a function of transistor sizes
- Need to reduce C_L , V_{dd} and f to reduce power.


Digital Integrated Circuits

Inverter

© Prentice Hall 1995

Dissipation Due to Direct-Path Currents

 - during switching the NMOS and the PMOS transistors are conducting simultaneously.
- This puts the power supply in "short-circuit" during the transitions of the input signal
- "short-circuit" current is limited by transistors current capacity \Rightarrow depends on transistor size



Digital Integrated Circuits

Inverter


© Prentice Hall 1995

Dissipation Due to Direct-Path Currents

t_{sc} : shot circuit duration

$$t_{sc} = \frac{V_{DD} - 2V_T}{V_{DD}} t_s = \frac{V_{DD} - 2V_T}{V_{DD}} \times \frac{t_{r(f)}}{0.8}$$

 $t_{r(f)}$: rise (fall) time of input signal (10%-90%)



$$E_{dp} = V_{DD} \frac{I_{peak} t_{sc}}{2} + V_{DD} \frac{I_{peak} t_{sc}}{2} = t_{sc} V_{DD} I_{peak}$$

$$P_{dp} = t_{sc} V_{DD} I_{peak} f$$

I_{peak} : peak current of transistors ($V_O = V_{DD}/2$)

f : switching frequency


Digital Integrated Circuits

Inverter

© Prentice Hall 1995

Dissipation Due to Leakage

 - reverse-biased diode junctions and transistors leakage
- 10-100 pA/ μm^2 at room temperature.
- Increases exponentially with temperature



$$P_{stat} = I_{stat} V_{DD}$$

I_{stat} : leakage currents

Digital Integrated Circuits

Inverter

© Prentice Hall 1995

Total Power Dissipation

$$P_{tot} = P_{dyn} + P_{dp} + P_{stat}$$

$$P_{tot} = (C_L V_{DD}^2 + V_{DD} I_{peak} t_s) f_0 + V_{DD} I_{leak}$$

• Low frequency operation: P_{stat} dominates

• High frequency operation: $P_{dyn} + P_{dp}$ dominates

Digital Integrated Circuits

Inverter

© Prentice Hall 1995